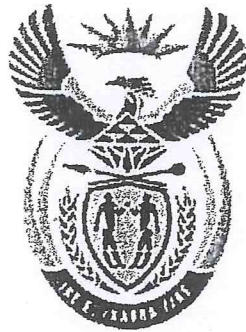


201208153



# higher education & training

---

Department:  
Higher Education and Training  
REPUBLIC OF SOUTH AFRICA

T780(E)(A1)T  
AUGUST 2012

NATIONAL CERTIFICATE

**INDUSTRIAL ELECTRONICS N1**

(8080641)

**1 August (X-Paper)**  
**09:00 – 12:00**

**This question paper consists of 6 pages and a formula sheet.**



**DEPARTMENT OF HIGHER EDUCATION AND TRAINING  
REPUBLIC OF SOUTH AFRICA**

**NATIONAL CERTIFICATE  
INDUSTRIAL ELECTRONICS N1**

**TIME: 3 HOURS**

**MARKS: 100**

---

**INSTRUCTIONS AND INFORMATION**

1. Answer ALL the questions.
  2. Read ALL the questions carefully.
  3. Number the answers correctly according to the numbering system used in this question paper.
  4. Write neatly and legibly.
-

**QUESTION 1**

1.1 Choose a/an word/item from COLUMN B that matches a description in COLUMN A. Write only the letter (A – N) next to the question number (1.1.1 – 1.1.10) in the ANSWER BOOK.

COLUMN A		COLUMN B
1.1.1	Blocks direct current	A an inductor
1.1.2	Is assembled from one piece of N-material and one piece of P-material	B a bridge rectifier C a transistor
1.1.3	Is the number of cycles which pass a given point in one second	D a diode E a full-wave rectifier
1.1.4	Is shared in a series resistor circuit	F voltage G frequency
1.1.5	It is the tolerance of a gold colour band	H a transformer
1.1.6	Is assembled using two diodes	I 5% J 10%
1.1.7	Can be used as an electronic switch	K 0,6 - 0,7 V
1.1.8	Possesses an ability to oppose any change in the existing current	L 0,2 - 0,3 V M positive
1.1.9	The junction voltage of a silicon diode	N negative
1.1.10	The charge on a hole	

(10 × 1) (10)

1.2 A 12-volt radio draws a current of 15 mA.

Calculate the following:

1.2.1 The power dissipated by the radio (3)

1.2.2 The minimum resistance of the radio (3)

1.3 Make a sketch of a bar magnet and show the magnetic lines of force and their direction around the bar magnet. (4)

- 1.4 State the left-hand rule for solenoids/coils. (3)
  - 1.5 State the law of magnetism with respect to bar magnets. (2)
- [25]

**QUESTION 2**

- 2.1 Name the units in which each of the following is measured:
  - 2.1.1 Electromotive force (1)
  - 2.1.2 A charge (1)
  - 2.1.3 Frequency (1)
  - 2.1.4 Resistance temperature coefficient (1)
  - 2.1.5 Inductance (1)
- 2.2 Sketch the IEC symbols for each of the following components:
  - 2.2.1 An inductor with a ferrite core (1)
  - 2.2.2 An NPN transistor (1)
  - 2.2.3 A pre-set capacitor (1)
  - 2.2.4 A cell (1)
  - 2.2.5 A saw-tooth wave (1)

2.3 Refer to FIGURE 1 below and calculate the following:

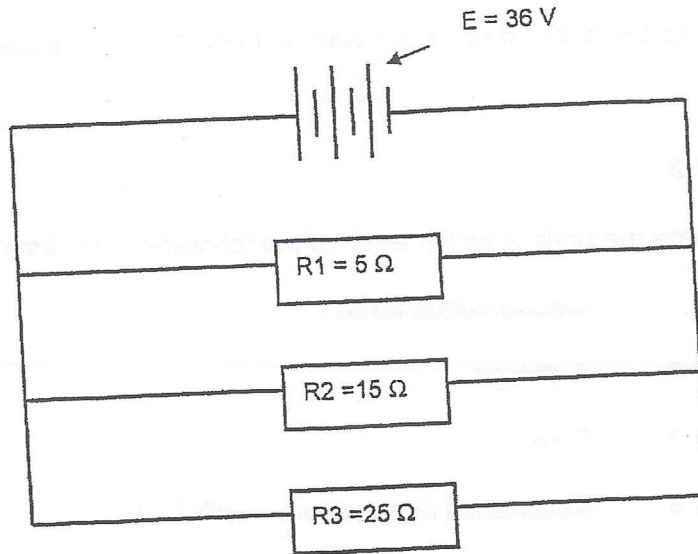


FIGURE 1

- 2.3.1 The total resistance in the circuit (5)
- 2.3.2 The total current flow through the circuit (3)
- 2.3.3 The voltage drop across R2 (1)
- 2.3.4 The current flow through R2 (3)
- 2.3.5 The power dissipated by R2 (3)

[25]

QUESTION 3

- 3.1 State FOUR factors that influence the resistance of a conductor. (4)
- 3.2 State THREE factors that influence the capacitance of a capacitor. (3)
- 3.3 State FOUR factors that determine the magnitude of an induced EMF in the conductor. (4)
- 3.4 Calculate the resistance of a 65-m long copper conductor with a cross sectional area of  $28 \times 10^{-6}\text{ mm}^2$ . The resistivity of copper is 1,7 micro-ohm metres. (3)
- 3.5 A tube filled with mercury has a resistance of  $23\ \Omega$  at  $0\ ^\circ\text{C}$ . If the tube is heated up to  $45\ ^\circ\text{C}$ , what will be its resistance? Take the resistance temperature coefficient of the tube as  $0,0042\ \Omega/^\circ\text{C}$ . (3)

3.6 A transformer with a supply voltage of 220 V has a turns ratio of 2:1.

Calculate the following:

3.6.1 The secondary voltage (4)

3.6.2 The secondary current if the primary current is 20 mA (4)


[25]

**QUESTION 4**

4.1 Indicate the following voltage readings for the circuit diagram below:

4.1.1 Across the silicon diode (2)

4.1.2 Across the lamp (2)

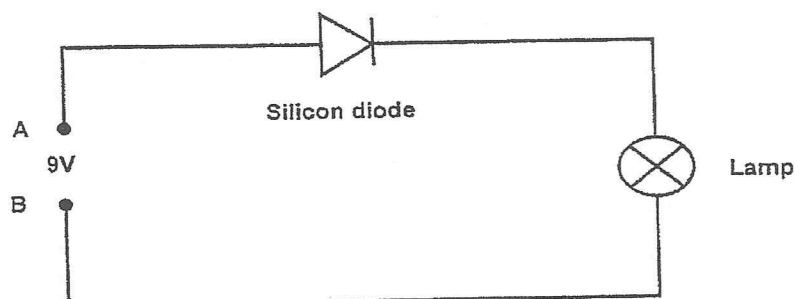

**FIGURE 2**

4.2 How many valence electrons does a germanium atom have? (1)

4.3 Explain what is meant by *covalent bond*. (2)

4.4 Explain the conditions under which a diode will conduct/pass current with respect to the polarity of the anode and the applied voltage. (4)

4.5 Name TWO types of multimeters. (2)

4.6 Define the term *induction*. (2)

4.7 Define the term *potential difference*. (3)

4.8 Make a neat, labelled sketch of a discharging curve for a capacitor. (3)

4.9 Make a neat, labelled sketch of a full-wave bridge rectifier circuit. (4)

[25]

**TOTAL: 100**





**INDUSTRIAL ELECTRONICS N1****FORMULA SHEET**

$$I = \frac{V}{R}$$

$$I = \frac{E}{R + r}$$

$$P = V \times I$$

$$R_t = R_1 + R_2 + \dots + R_n$$

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

$$C_t = C_1 + C_2 + \dots + C_n$$

$$\frac{1}{C_t} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$

$$Q = C \times V$$

$$L_t = L_1 + L_2 + \dots + L_n$$

$$\frac{1}{L_t} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$

$$\frac{V_p}{V_s} = \frac{N_p}{N_s} = \frac{I_s}{I_p}$$

$$R_t = R_o(1 + \alpha_o t)$$

$$R = \frac{\rho \ell}{A}$$

